

Decimator in PSoC®

AN51352

Author: Archana Yarlagadda

Associated Project: No

Associated Part Family: CY8C24x94, CY8C27x43, CY8C29x66,

CY8C23x33, CY8C24x23A Software Version: None

Associated Application Notes: AN2010, AN2041, AN2239

Application Note Abstract

This application note describes the decimator, which is a hardware block used in Delta-Sigma and incremental ADCs in PSoC®. It discusses density signals, decimation functions, and Sinc filters, and how they are related to the decimator in PSoC.


Introduction

The decimator is an important hardware function in the implementation of Delta-Sigma and incremental Analog-to-Digital Convertors (ADCs) in PSoC. A decimator is a digital Finite Impulse Response (FIR) filter that converts a density stream into parallel digital data. The decimator is chosen over other external FIR filters in PSoC because of its simplicity in implementation and cost effectiveness in silicon area. This application note assumes that you are familiar with user modules (UM) in PSoC. If you are new to PSoC, refer the application note AN2010, *Getting Started with PSoC*.

Density Domain

Density is the percentage of '1's in the digital signal stream of '1's and '0's. The percentage in the signal that is high is important and not the particular waveform. From the density perspective, all the signals shown in Figure 1 are equivalent.

Figure 1. 50% Density Waveforms

 

The density signal is a digital signal interpreted in density domain. The benefits of signal processing in the density domain are:


- Simple logic gates
- Higher immunity to noise
- Better resolution at lesser logic blocks, unlike digital signal processing

Density Signal in PSoC

A modulator converts either an analog or a digital value to a density signal. In this application note, the focus is on the analog modulators, because decimators are used in the ADCs in PSoC.


An example of an analog modulator is a Delta Sigma Modulator (DSM). The DSM is a combined integrator and comparator formed with a switched capacitor block. A DSM is a part of the DelSig ADC UM, where the analog signal is converted into a density signal by the modulator and fed into the decimator, as shown in Figure 2.

Figure 2. Block Diagram of DelSig ADC

 

The density signal is observed in the ADCs by connecting the comparator bus output to a digital buffer (DigBuf) UM, and connecting it to an output port pin (Figure 3).

Figure 3. Routing the Comparator Bus to Output Port

 


A DSM is formed with the switched capacitor block (SCBlock) UM in PSoC with the parameter settings shown in Figure 4. The output density signal is observed by connecting to the output pin shown in Figure 3. Refer to AN2041 for more information about switched capacitor analog blocks.

Figure 4. SCBlock Settings that Implement a DSM

roperties - SCBLOCK_1				
Name	SCBLOCK_1			
User Module	SCBLOCK			
Version	2.4			
FCap	32			
ClockPhase	Norm			
ASign	Pos			
ACap	16			
AMux	ACB00			
BCap	0			
AnalogBus	AnalogOutBus_1			
CompBus	ComparatorBus_1			
AutoZero	On			
ССар	0			
ARefMux	ComparatorBus_1			
FSW1	On			
FSW0	Off			
BSW	Off			
BMux	ACB01			
Power	High			

Figure 5 shows an example of the density signal output from an analog modulator. The output signal for the reference from 0 to 5V is shown. It is not the shape of the waveform that matters in the density domain, but the percentage of '1's in the waveform.

Figure 5. Inputs and Outputs of Analog Modulator

 

The DSM is an oversampled converter. This implies that the output bit-stream of the modulator is at a higher rate than the required Nyquist frequency. Therefore, the quantization noise is lower in the bandwidth of interest and the noise increases rapidly beyond the bandwidth. Thus, we need a hardware function that accomplishes two goals:


- Downsampling To reduce the sample rate to the Nyquist rate
- Filtering To eliminate the out of band noise

In the decimator, these functions are performed with decimation and a Sinc^2 filter. This is described in the following sections.

Decimation

Decimation is a function that downsamples the input signal. It has the benefits of higher signal to noise ratio and lower power consumption. It is an averaging function that accumulates N bits and averages them to give an output value. Decimation for digital signals is similar to sampling for analog signals. The most economical method of implementation of a decimation function is to pick one sample out of K samples. This is the method used in PSoC, by use of a hold register and clocking it at the decimation frequency. Considering an input signal B with frequency $f_{\rm s}$, the output of the decimation register is a signal C, with frequency $f_{\rm d}$, as shown in Figure 6.


Figure 6. Decimation Function with Hold Register

 

Sinc Filter

A Sinc filter is a low pass digital filter that attenuates the quantization, interference, and anti-aliasing noise. The Sinc filter gets its name from the frequency response of the filter that is of the form $\sin(\omega)/(\omega)$. Filtering in the density domain does not need any digital multipliers. It can be implemented easily by cascading accumulators and differentiators. The block diagram for the Sinc filter is shown in Figure 7 and a description of each block follows.

Figure 7. Block Diagram for Decimator Sinc Filter

 

Accumulation

The accumulator is implemented using adders and delay blocks. For an input signal A(n) and accumulated signal B(n), accumulation in time domain is represented by Equation 1.

$$B(n) = B(n-1) + A(n)$$
 Equation 1


In Z domain it translates to:

$$B(z) = B(z)z^{-1} + A(z)$$
 Equation 2

$$H(z) = \left[\frac{1}{1 - z^{-1}}\right]$$
 Equation 3

The Z domain representation for the transfer function obtained in Equation 3 is given in Figure 8.

Figure 8. Transfer Function for Accumulator

 

Differentiation

The differentiator is implemented using subtraction and delay blocks. In time domain, when the delay is K, differentiation is represented by Equation 4.

$$D(n) = C(n) - C(n - K)$$
 Equation 4


In Z domain it translates to

$$D(z) = C(z) - C(z)z^{-K}$$
 Equation 5

$$H(z) = 1 - z^{-K}$$
 Equation 6


The Z domain representation for the transfer function obtained in Equation 6 is given in Figure 9.

Figure 9. Transfer Function for Differentiator

 

When the Sinc function is applied twice, we get a $\rm Sinc^2$ filter that has lower cut off frequency and better noise elimination. The graph of a Sinc function and a $\rm Sinc^2$ function for $\rm f_s$ =125 kHz is shown in Figure 10. The $\rm Sinc^2$ response is for a decimation rate of K=32. The equation used to plot the $\rm Sinc^2$ function is described in detail in the next section. The graph in Figure 10 explains why a $\rm Sinc^2$ filter is chosen for PSoC, with more clarity.

Figure 10. Comparison of Sinc vs Sinc² Function

 


Decimator in PSoC

As mentioned earlier, the decimator is a digital filter that has the Sigma (accumulation) – Delta (differentiation) functionality. The decimator in PSoC has the Sinc² filter and decimation function incorporated in it, to form a Sinc² decimation filter. The decimation rate is also the rate at which differentiation is performed. A Sinc² filter is obtained by applying the Sinc function twice—by cascading two accumulators and two differentiators.

The complete block diagram of the decimator, formed with the blocks discussed in the previous section and a decimation rate of K is shown in Figure 11. This is the block diagram of a Type 2 decimator in PSoC, which has the complete decimation operation in hardware. There are other forms of decimators in PSoC and their differences from this base module are given in a later section.

Figure 11. Block Diagram for Decimator showing Accumulation, Decimation, and Differentiation

 

Considering the accumulator and differentiator equations (Equation 3 and Equation 6), and the decimation function, the normalized transfer function of the decimator for a Sinc² decimation filter is given by Equation 7.

$$H(z) = \left[\frac{1}{K} \frac{1 - z^{-K}}{1 - z^{-1}} \right]^2$$
 Equation 7

The frequency response of this normalized transfer function is given in Equation 8. It is this equation that is plotted in Figure 10 and compared with the Sinc function that has the $\sin(\omega)/(\omega)$ format.

$$H(e^{j\omega}) = \left(\frac{1}{K} \frac{\sin\left(\frac{\pi f K}{f_s}\right)}{\sin\left(\frac{\pi f}{f_s}\right)}\right)^2$$
 Equation 8

In the case of a DelSig UM, the accumulation is performed at the same frequency as the modulation (Equation 9). In one DataClk cycle, both the accumulations are completed, the first accumulation during $\phi 1$ and the second during $\phi 2$.


$$f_s = \frac{DataClk}{4}$$
 (Same as ϕ_1 and ϕ_2) Equation 9

The differentiators operate at a lower frequency, depending on the decimation rate. If the decimation rate is K, then the decimation register and differentiators are clocked at frequency f_d given by Equation 10.

$$f_d = \frac{DataClk}{4*K}$$
 Equation 10

The output of the decimator is N bit data that comes out at frequency $f_{\rm d}.$ The output of the decimator is shown in Figure 12. To avoid overflow during internal calculations, the internal registers and the bus lines have a higher number of bits than the maximum resolution. The data is shifted based on the resolution bits parameter and the output is stored in registers DEC_DH and DEC_DL in PSoC. The data value is later processed in the interrupt service routine (ISR). The data processing can be a function such as conversion from unsigned to signed, because the hardware treats the data as unsigned.

Figure 12. Inputs and Outputs of Decimator

 

Types of Decimators in PSoC

In PSoC, there are both Type 1 and Type 2 decimators.

Type 1 Decimator Block

The Type 1 decimator has the accumulation performed in the hardware and requires the differentiation in firmware. Also, the density signal is represented as '1's and '-1's instead of '1's and '0's. In other words, when the input is a '0', 1 is subtracted from the accumulated value. The PSoC device families that have a Type 1 decimator block are:

- CY8C27x43
- CY8C24x23A

Type 2 or Super Decimator Block

The Type 2 decimator has a full version of the Sinc² filter. Both the accumulation and decimation are performed in hardware and thus it is much faster and uses less memory.

- CY8C29x66: Uses an external digital block timer
- CY8C24x94: Can choose either external digital block or an internal timer

The decimator in the Delta Sigma ADC is a low pass filter. It is more complex than a counter, which is the most basic form of filter. The decimator block is also used in the Incremental ADC (ADCINC) UM as a digital counter block, and thus saves a digital block. In this mode, the decimator block is used in place of a counter to count the number of times the output is high. Other incremental ADCs such as ADCINC14, ADCINC12, and ADCINCVR have the same sample rate as ADCINC but they use a digital block for the counter. The decimator is used in both ADCINC and DELSIG ADC modules, but in different configurations, that results in differences between the two. For detailed information on the differences in ADCs refer application note AN2239, ADC Selection.

Summary

The decimator is a low pass digital filter. It converts a density bit stream into parallel digital data and reduces the noise on the input signal. The decimator is more efficient than a counter, which is the simplest of the low pass digital filters. In PSoC, the Delta Sigma ADCs use the decimator as a low pass Sinc² decimation filter. The incremental ADCs use the decimator in place of a counter, because it saves a digital block. Using decimators for filtering makes the signal processing in PSoC easier to implement, and less expensive in terms of silicon area.

About the Author

Name: Archana Yarlagadda

Title: Applications Engineer

Background: Masters in Analog VLSI from University

of Tennessee, Knoxville

Contact: yara@cypress.com

Document History

Document Title: Decimator in PSoC®

Document Number: 001-51352

Revis	on ECN	Orig. of Change	Submission Date	Description of Change
**	2678596	YARA	03/25/09	New application note

PSoC is a registered trademark of Cypress Semiconductor Corp. "Programmable System-on-Chip" and PSoC Designer are trademarks of Cypress Semiconductor Corp. All other trademarks or registered trademarks referenced herein are the property of their respective owners.

Cypress Semiconductor 198 Champion Court San Jose, CA 95134-1709 Phone: 408-943-2600 Fax: 408-943-4730 http://www.cypress.com/

© Cypress Semiconductor Corporation, 2009. The information contained herein is subject to change without notice. Cypress Semiconductor Corporation assumes no responsibility for the use of any circuitry other than circuitry embodied in a Cypress product. Nor does it convey or imply any license under patent or other rights. Cypress products are not warranted nor intended to be used for medical, life support, life saving, critical control or safety applications, unless pursuant to an express written agreement with Cypress. Furthermore, Cypress does not authorize its products for use as critical components in life-support systems where a malfunction or failure may reasonably be expected to result in significant injury to the user. The inclusion of Cypress products in life-support systems application implies that the manufacturer assumes all risk of such use and in doing so indemnifies Cypress against all charges.

This Source Code (software and/or firmware) is owned by Cypress Semiconductor Corporation (Cypress) and is protected by and subject to worldwide patent protection (United States and foreign), United States copyright laws and international treaty provisions. Cypress hereby grants to licensee a personal, non-exclusive, non-transferable license to copy, use, modify, create derivative works of, and compile the Cypress Source Code and derivative works for the sole purpose of creating custom software and or firmware in support of licensee product to be used only in conjunction with a Cypress integrated circuit as specified in the applicable agreement. Any reproduction, modification, translation, compilation, or representation of this Source Code except as specified above is prohibited without the express written permission of Cypress.

Disclaimer: CYPRESS MAKES NO WARRANTY OF ANY KIND, EXPRESS OR IMPLIED, WITH REGARD TO THIS MATERIAL, INCLUDING, BUT NOT LIMITED TO, THE IMPLIED WARRANTIES OF MERCHANTABILITY AND FITNESS FOR A PARTICULAR PURPOSE. Cypress reserves the right to make changes without further notice to the materials described herein. Cypress does not assume any liability arising out of the application or use of any product or circuit described herein. Cypress does not authorize its products for use as critical components in life-support systems where a malfunction or failure may reasonably be expected to result in significant injury to the user. The inclusion of Cypress' product in a life-support systems application implies that the manufacturer assumes all risk of such use and in doing so indemnifies Cypress against all charges.

Use may be limited by and subject to the applicable Cypress software license agreement.